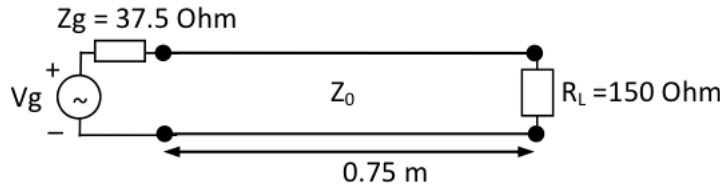


1. In the transmission-line circuit shown below the voltage at the load is $V_L = j5$ V and the operating frequency is 300 MHz. Given that the line is lossless of characteristic impedance of $150\ \Omega$ with wave velocity 3×10^8 m/s, calculate the following:

- The time-average power dissipated at the load;
- The time-average power delivered by the generator.



2. A TL with characteristic impedance $Z_o = 25\ \Omega$ and length $l = 0.15\lambda$ is terminated with a load $Z_L = 100\ \Omega$.

- Using a SC, determine (i) the load reflection coefficient Γ_L , (ii) the generalized reflection coefficient $\Gamma(d)$ at $d = l$, and (iii) the input impedance $Z(l)$ at the generator end. Hand in your S.C.

Hint: you start by entering $z_L = \frac{Z_L}{Z_o}$ in the SC. Express Γ_L and $\Gamma(l)$ as complex numbers in polar form — i.e, as $|\Gamma|\angle\theta$.

- Using $Z(l)$ from part (a), determine the voltage phasor $V(l)$ at the generator end if the generator has an open circuit voltage phasor $V_g = 8$ V and a Thevenin impedance $Z_g = 50\ \Omega$.
- Given the result of (b), determine V^+ such that $V(d) = V^+(e^{j\beta d} + \Gamma_L e^{-j\beta d})$.
- What is the load voltage phasor $V(0)$ given the result of (c)?
- What is the corresponding load current $I(0)$?

3. A TL with characteristic impedance $Z_o = 50\ \Omega$ and length $l = 0.4\lambda$ has an *open* termination at $d = 0$ and a $50\ \Omega$ resistor connected between the TL conductors (a “shunt” connection) at $d = 0.2\lambda$. Use a SC to determine the input impedance and admittance of the line at the generator end, i.e., $Z(l)$ and $Y(l)$. Hand in your marked SC.

Hint: first move by 0.2λ from the load point (where you enter $z(0)$ or $y(0)$) toward generator on the SC, read off the corresponding $y(d)$, combine it in parallel with the shunt element, go back onto the SC with the normalized combined admittance, and move another 0.2λ toward the generator...

- Two TL stubs of equal lengths $l = 0.35\lambda$ and identical short terminations have unequal characteristic impedances of $Z_o = 50\ \Omega$ and $100\ \Omega$. If the two stubs are connected in parallel at their input ports, what is the input admittance of the combined network? Use a SC to solve this problem and hand in your marked SC.
- A transmission line having a characteristic impedance of $50\ \Omega$ is terminated by a load of unknown impedance Z_L . Measurements of the voltage amplitude $|V(d)|$ along the line reveal a “standing wave pattern” with a maximum voltage of 7.2 V and a minimum voltage of 1.8 V.
 - What is the voltage standing wave ratio (VSWR) on the line?

- b) A voltage minimum is observed at distance $d = 2.287\lambda$ from the load. What is then the distance d_{min} between the load and the first voltage minimum (closest to the load)? Hint: successive voltage minima are $\frac{\lambda}{2}$ apart.
- c) Determine the magnitude and phase angle of the load reflection coefficient Γ_L using the S.C. and the results of parts (a) and (b). **Hint:** Given the VSWR, constant- Γ circle passes through $z = \text{VSWR} + j0$ on the S.C. The same location on the S.C. also correspond to the location of a voltage maximum on the line.
- d) Determine z_L using the S.C. and the value Z_L in Ω 's.
- e) Determine $|V^+|$ and $|V^-|$, the travelling wave amplitudes on the line.
- f) What is the average power (in W) delivered to the load?
6. We want to use a quarter-wave transformer to match a load Z_L to a T.L. with a characteristic impedance $Z_o = 25\Omega$. The quarter wave transformer is to be inserted at a distance d_1 away from the load.
- a) Determine d_1 (in units of λ) and the characteristic impedance Z_{qo} of the quarter wave transformer if
- $Z_L = 100\Omega$,
 - $Z_L = 100 + j100\Omega$.
- b) For $Z_L = 100 + j100\Omega$, what is VSWR in the region
- $0 < d < d_1$,
 - $d_1 < d < d_1 + \frac{\lambda}{4}$,
 - $d_1 + \frac{\lambda}{4} < d$
7. We want to use a single-stub tuner to match a load Z_L to a T.L. with a characteristic impedance $Z_o = 100\Omega$. A shorted-stub is to be connected at a distance d_1 away from the load.
- a) Determine d_1 (in units of λ) and the length d_s of the shorted stub if $Z_L = 50 + j50\Omega$ and the characteristic impedance of the stub is 100Ω .
- b) Repeat (a) if the characteristic impedance of the stub is 50Ω .