
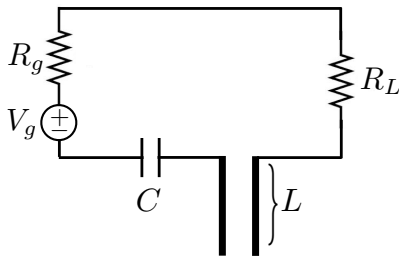


- Consider a lossless TL which is short circuited at both ends. If  $l = 5$  m is the length of the line, and  $v = \frac{1}{3}c = 10^8$  m/s for the line,
  - What are all the resonance frequencies of the line — frequencies at which source-free *oscillations* (standing waves) of voltage and current are sustained on the line — expressed in MHz units?  
**Hint:** to satisfy the “open” boundary conditions at both ends of the line, we want the current phasor to vanish at  $z = 0$  and  $z = l$  when the oscillation frequency is resonant.
  - Sketch the shapes of current magnitude  $|I(z)|$  vs  $z$  for the line corresponding to the *three lowest resonance frequencies*. Label each plot clearly and explain each briefly.
  - Repeat (b) for voltage magnitude  $|V(z)|$  vs  $z$ .
- Consider the circuit shown below, where a resistor,  $R_L = 50 \Omega$ , and a capacitor  $C$ , are connected in series with an open-circuited transmission line stub with characteristic impedance  $Z_0 = R_L$ ,  $v = c$ , and length  $L = 160$  cm (see diagram).

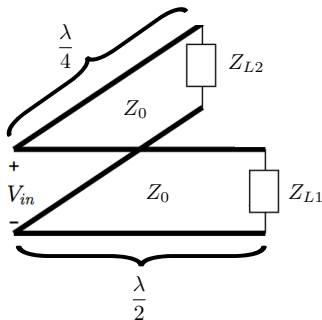


- What is the input impedance,  $Z(L)$ , of the open T.L. stub?
  - The circuit is driven by a voltage source of magnitude  $V_g$  at a frequency of 50 MHz, which has internal resistance  $R_g = R_L$ . If the voltage at the load,  $V_L$ , equals  $V_g/2$ , what is the capacitance  $C$ ?
- Two transmission line segments each having characteristic impedance  $Z_0 = 100 \Omega$  are connected in parallel and share input voltage  $V_{in} = j10$  V. One transmission line has electrical length  $l = \frac{\lambda}{2}$  and is terminated by a resistive load  $Z_{L1} = 200 \Omega$ , while the other has electrical length  $l = \frac{\lambda}{4}$  is terminated by  $Z_{L2} = 50 \Omega$ .



- What is the voltage  $V_{L1}$  across  $Z_{L1}$ ?
- What is the voltage  $V_{L2}$  across  $Z_{L2}$ ?
- What is the current  $I_{L1}$  through  $Z_{L1}$ ?

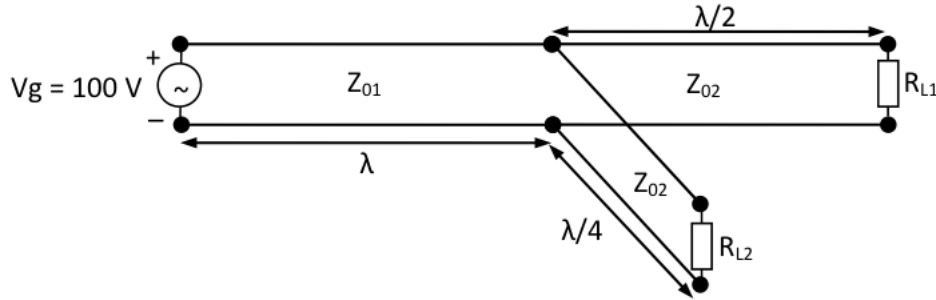- d) What is the current  $I_{L2}$  through  $Z_{L2}$ ?
- e) What is the input impedance  $Z_{in}$  associated with the combined TL network?
- f) What is the total time-averaged power absorbed by the two resistive loads?
4. A quarter-wavelength long transmission line section having characteristic impedance  $Z_o = 100 \Omega$  is terminated by an unknown impedance  $Z_L$  at one end. The input current phasor at the other end is  $I_{in} = 0.5 \angle 0^\circ$  A. Let  $V_{in}$  and  $V_L$  denote input and load voltage phasors, respectively, with directions defined in a compatible way with one another and with  $I_{in}$ .
- a) Assuming that the load is not shorted (i.e.,  $Y_L = \frac{1}{Z_L} \neq 0$ ) what is  $V_L$ ?
- b) Is it possible for  $I_{in} = 0.5 \angle 0^\circ$  A if the load is a short? Discuss your answer.
- c) What is  $V_{in}$  if  $Z_L = 50 \Omega$ ?
5. In the transmission-line circuit shown below all lines are lossless,  $Z_{01} = 2Z_{02} = 100 \Omega$  and  $R_{L1} = R_{L2} = 50 \Omega$ . Calculate the following:
- a) Voltage and current phasors at the two loads,
- b) Time-average power dissipated at the two loads.



6. Consider a lossless TL having electrical length  $l = \lambda$ , characteristic impedance  $Z_0 = 50 \Omega$ , propagation velocity  $v = c$ , and resistive load  $Z_L = 150 \Omega$ . The TL is connected in series with an open circuit voltage source  $V_g = 30e^{-j\frac{\pi}{2}}$  V having Thevenin impedance  $R_g$ , and the voltage across the load  $Z_L$  is known to be  $V_L = -j10$  V.
- a) What is  $I_L$ ?
- b) At what distance(s)  $d$  along the TL (where  $d = 0$  at the load end) is the line impedance  $Z(d) = Z_L$ ?
- c) What is  $V(d = \frac{\lambda}{4})$  and  $I(d = \frac{\lambda}{4})$ ?
- d) What is  $Z(d = \frac{\lambda}{4})$ ?
- e) What is  $V(d = \frac{\lambda}{2})$  and  $I(d = \frac{\lambda}{2})$ ?
- f) What is  $R_g$ , the Thevenin impedance of the generator?