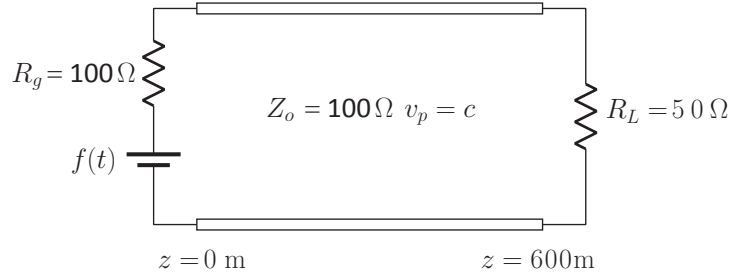


1. Let us consider a T.L. with characteristic impedance  $Z_o = 100 \Omega$ , length  $l = 600 \text{ m}$ , and propagation velocity  $v_p = c = 3 \times 10^8 \text{ m/s}$ . A voltage source  $f(t)$  with internal resistance  $R_g = Z_o$  is connected at  $z = 0$  and a load resistance  $R_L = Z_o/2$  is placed at  $z = l$  as shown in the following diagram.



- a) For  $f(t) = \delta(t)$ , the initial voltage at the input of the T.L. is given by the voltage divider

$$\frac{Z_o}{R_g + Z_o} \delta(t) = \frac{1}{2} \delta(t).$$

In addition, the voltage reflection coefficients at the source-end and at the load-end are

$$\Gamma_{Vg} = \frac{R_g - Z_o}{R_g + Z_o} = \frac{100 - 100}{100 + 100} = 0 \quad \text{and} \quad \Gamma_{VL} = \frac{R_L - Z_o}{R_L + Z_o} = \frac{50 - 100}{50 + 100} = -\frac{1}{3},$$

respectively. The corresponding current reflection coefficients are

$$\Gamma_{Cg} = -\Gamma_{Vg} = 0 \quad \text{and} \quad \Gamma_{CL} = -\Gamma_{VL} = \frac{1}{3}.$$

Using these information, we can build the following "bounce diagrams" for the voltage  $V(z, t)$  and current  $I(z, t)$  on the transmission line.

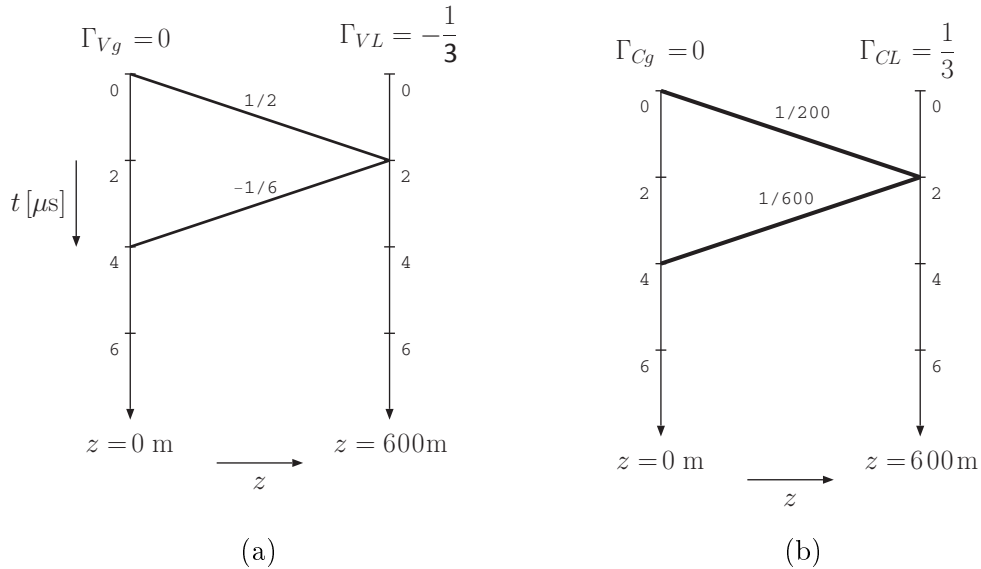


Figure 1: (a) Voltage and (b) current bounce diagrams for voltage source  $f(t) = \delta(t)$ .

- b) The expressions for  $V(z, t)$  and  $I(z, t)$  are

$$V(z, t) = \frac{1}{2} \delta\left(t - \frac{z}{c}\right) - \frac{1}{6} \delta\left(t + \frac{z}{c} - 4\mu\text{s}\right)$$

$$I(z, t) = \frac{1}{200} \delta\left(t - \frac{z}{c}\right) + \frac{1}{600} \delta\left(t + \frac{z}{c} - 4\mu\text{s}\right).$$

Evaluating these expressions at  $z = \frac{l}{4} = 150 \text{ m}$ , we have

$$\begin{aligned} V(\frac{l}{4}, t) &= \frac{1}{2}\delta(t - 0.5\mu\text{s}) - \frac{1}{6}\delta(t - 3.5\mu\text{s}) \\ I(\frac{l}{4}, t) &= \frac{1}{200}\delta(t - 0.5\mu\text{s}) + \frac{1}{600}\delta(t - 3.5\mu\text{s}). \end{aligned}$$

c) According to the previous result, the impulse voltage response at  $z = \frac{l}{4}$  is

$$h_v(t) = \frac{1}{2}\delta(t - 0.5\mu\text{s}) - \frac{1}{6}\delta(t - 3.5\mu\text{s}).$$

Therefore, if the source voltage is  $f(t) = 10u(t) \text{ V}$ , we can compute  $V(\frac{l}{4}, t)$  as follows

$$V(\frac{l}{4}, t) = f(t) * h_v(t) = 5u(t - 0.5\mu\text{s}) - \frac{5}{3}u(t - 3.5\mu\text{s}) \text{ V}.$$

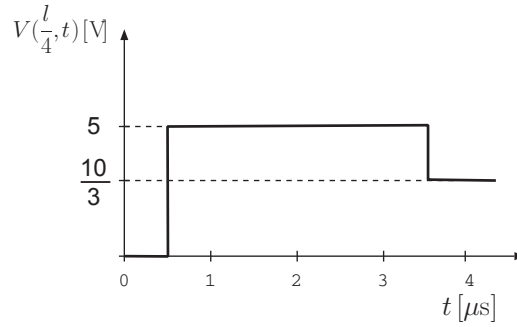


Figure 2: Voltage as function of time at  $z = \frac{l}{4}$  for voltage source  $f(t) = 30u(t)$ .

d) We know that

$$\begin{aligned} V(z, t) &= \frac{1}{2}\delta(t - \frac{z}{c}) - \frac{1}{6}\delta(t + \frac{z}{c} - 4\mu\text{s}) \\ I(z, t) &= \frac{1}{200}\delta(t - \frac{z}{c}) + \frac{1}{600}\delta(t + \frac{z}{c} - 4\mu\text{s}). \end{aligned}$$

Now, if the source voltage is  $f(t) = 10u(t) \text{ V}$ , we can compute  $V(z, t)$  and  $I(z, t)$  as follows

$$\begin{aligned} V(z, t) &= 5u(t - \frac{z}{c}) - \frac{5}{3}u(t + \frac{z}{c} - 4\mu\text{s}) \text{ V} \\ I(z, t) &= \frac{1}{20}u(t - \frac{z}{c}) + \frac{1}{60}u(t + \frac{z}{c} - 4\mu\text{s}) \text{ A}. \end{aligned}$$


Therefore, by plotting  $V(z, t)$  and  $I(z, t)$  as a function of time, we can easily find the steady state values as

$$V(z, t) = 5 - \frac{5}{3} = \frac{10}{3} \text{ V} \quad \text{and} \quad I(z, t) = \frac{1}{20} + \frac{1}{60} = \frac{1}{15} \text{ A}.$$

2. Let us consider the following circuit diagram where  $Z_o$ ,  $R_L$ , and  $L$  are unknowns.

- According to the voltage waveform plotted above, the incident pulse has an amplitude of  $60 \text{ V}$ . Since the ratio between this amplitude and the source voltage is given by the voltage divider formula  $\tau_g = \frac{Z_o}{Z_o + 50} = \frac{60}{90} = \frac{2}{3}$ , we can find that  $Z_o = 100 \Omega$ .
- The amplitude of the first reflected pulse is  $-20 \text{ V}$ , therefore, the reflection coefficient at the load is  $\Gamma_L = -\frac{20}{60} = -\frac{1}{3}$ . Next, given that  $\Gamma_L = \frac{R_L - Z_o}{R_L + Z_o}$ , we can find that  $R_L = \frac{Z_o}{2} = 50 \Omega$ .

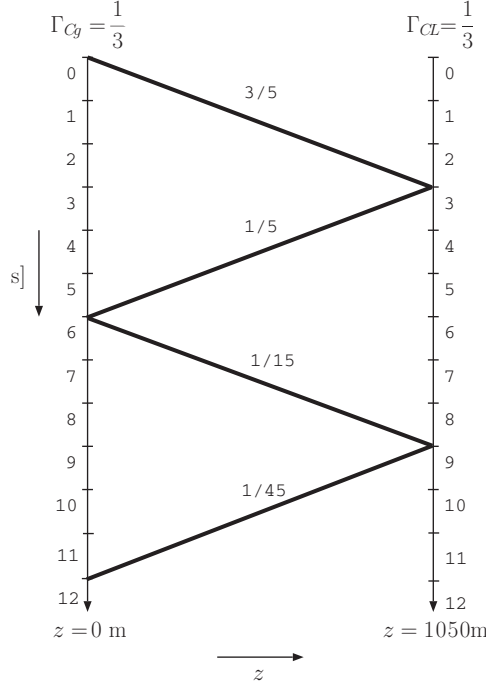- c) The time interval between the incident pulse and the second reflected pulse is  $6\mu\text{s}$ , since this time is equal to the two-way travel time, we have that the time it takes the pulse to travel from one end of the line to the other is  $T = \tau_L = 3\mu\text{s}$ .
- d) Since at  $z = 300\text{ m}$ , the incident pulse is delayed by  $2\mu\text{s}$ , the propagation speed is  $v_p = \frac{300\text{ m}}{2\mu\text{s}} = 150 \times 10^6\text{ m/s}$ . Then, we can find that the length of the line is  $L = v_p \times \tau_L = 150 \times 3 = 450\text{ m}$ .
- e) The reflection coefficient at the source is  $\Gamma_g = -\frac{1}{3}$ . Therefore, the next two voltage impulses are  $-\frac{20}{9}\delta(t - 10)\text{ V}$  and  $\frac{20}{27}\delta(t - 14)\text{ V}$ .
- f) Bounce diagram for the current waveform  $I(z, t)$ .




- g) The expression for the current waveform for  $0 < z < L$  and  $0 < t < 12\mu\text{s}$  is

$$I(z, t) = \frac{3}{5}\delta(t - \frac{z}{v_p}) + \frac{1}{5}\delta(t + \frac{z}{v_p} - 6\mu\text{s}) + \frac{1}{15}\delta(t - \frac{z}{v_p} - 6\mu\text{s}) + \frac{1}{45}\delta(t + \frac{z}{v_p} - 12\mu\text{s})\text{ A}.$$

3. A system of two connected transmission lines is shown in the figure below. A switch is closed at  $t = 0$  and the positive voltages are measured for  $5\mu\text{s}$  giving the bounce diagram in the figure. Using these figures, we can identify and compute the following parameters of the circuit.

- a) Transmission time  $T_1 = 2\mu\text{s}$  and  $T_2 = 3\mu\text{s}$ .
- b)  $v_{p1} = \frac{400\text{ m}}{2\mu\text{s}} = 200 \times 10^6\text{ m/s}$  and  $v_{p2} = \frac{300\text{ m}}{3\mu\text{s}} = 100 \times 10^6\text{ m/s}$ .
- c) Since there is no reflection at the load  $R_L$ , the characteristic impedance of line 2 is  $Z_2 = R_L = 60\Omega$ .
- d) At the interface, note that  $1 + \Gamma_{12} = \frac{40}{60} = \frac{2}{3}$ , thus the reflection coefficient from 1 to 2 is  $\Gamma_{12} = -\frac{1}{3}$ .
- e) Since  $\Gamma_{12} = \frac{Z_2 - Z_1}{Z_2 + Z_1} = -\frac{1}{3}$ , the characteristic impedance of line 1 is  $Z_1 = 2Z_2 = 120\Omega$ .
- f) The reflection coefficient at the source is  $\Gamma_S = \frac{12}{-20} = -\frac{3}{5}$ . Since  $\Gamma_S = \frac{R_g - Z_1}{R_g + Z_1}$ , the source resistance is  $R_g = \frac{1}{4}Z_1 = 30\Omega$ .
- g) The source voltage is  $V_o = 60\frac{R_g + Z_1}{Z_1} = 60\frac{30 + 120}{120} = 75\text{ V}$ .
- h) Reflected voltage  $V^{-+-} = -4\text{ V}$ .

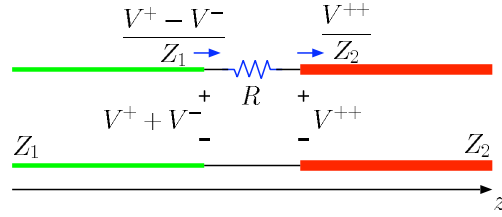- i) Since, as  $t \rightarrow \infty$ , transmission lines become ordinary wires, the steady-state voltage on line 1 is  $V_1 = V_o \frac{R_L}{R_g + R_L} = 75 \frac{60}{30+60} = 50 \text{ V}$ .
- j) Same as above, the steady-state voltage on line 2 is  $V_2 = 50 \text{ V}$ .
4. Let us consider two transmission lines with characteristic impedances  $Z_1$  and  $Z_2$  joined at a junction that includes a series resistance  $R$ .



- a) At the junction, on the side of the first line, the total voltage is equal to the sum of the incident voltage  $V^+$  plus the reflected voltage  $V^-$ . This total voltage is equal to the sum of the voltage across the resistor ( $V_R$ ) plus the voltage transmitted to the second line ( $V^{++}$ ). Thus, the KVL equation at the junction is

$$V^+ + V^- = V_R + V^{++}.$$

On the other hand, the current on the first line is equal to the sum of the incident current  $V^+/Z_1$  plus the reflected current  $-V^-/Z_1$ , therefore, the total current is  $(V^+ - V^-)/Z_1$ . This current is equal to the current flowing through the resistor ( $V_R/R$ ) and it is also equal to the current transmitted to the second line ( $V^{++}/Z_2$ ). Thus, the KCL equation at the junction is

$$\frac{V^+}{Z_1} - \frac{V^-}{Z_1} = \frac{V_R}{R} = \frac{V^{++}}{Z_2}.$$

- b) Combining the previous equations by eliminating  $V^{++}$  and  $V_R$  we have

$$\frac{V^+}{Z_1} - \frac{V^-}{Z_1} = \frac{V^+ + V^-}{R + Z_2} \rightarrow \left( \frac{1}{Z_1} - \frac{1}{Z_{eq}} \right) V^+ = \left( \frac{1}{Z_1} + \frac{1}{Z_{eq}} \right) V^-,$$

where  $Z_{eq} = R + Z_2$ . Thus, the reflection coefficient is

$$\Gamma_{12} = \frac{V^-}{V^+} = \frac{Z_{eq} - Z_1}{Z_{eq} + Z_1},$$

Similarly, but eliminating  $V^-$  and  $v_R$ , we have

$$\frac{V^+}{Z_1} - \frac{V^{++}(R + Z_2)/Z_2 - v^+}{Z_1} = \frac{V^{++}}{Z_2} \rightarrow \frac{2}{Z_1} V^+ = \left( \frac{R + Z_2}{Z_1 Z_2} + \frac{1}{Z_2} \right) V^{++}.$$

Therefore, the transmitted coefficient is

$$\tau_{12} = \frac{V^{++}}{V^+} = \frac{2Z_2}{R + Z_1 + Z_2}.$$

- c) Considering  $Z_1 = 50 \Omega$ ,  $Z_2 = 25 \Omega$ , and  $R = 100 \Omega$ , we can find that  $Z_{eq} = 125 \Omega$ . Then, we calculate

$$\Gamma_{12} = \frac{Z_{eq} - Z_1}{Z_{eq} + Z_1} = \frac{125 - 50}{125 + 50} = \frac{3}{7},$$

and

$$\tau_{12} = \frac{2Z_2}{R + Z_1 + Z_2} = \frac{2 \times 25}{100 + 50 + 25} = \frac{2}{7}.$$

Note that in this case  $1 + \Gamma_{12} \neq \tau_{12}$ .

5. We will solve as follows:

- a) The injection coefficient can be read directly from the plot as  $\tau_g = 0.5$  (because  $V_{input}(t) = \tau_g u(t) \Rightarrow V_{input}(t) = \tau_g$ ). Also, we know

$$\tau_g = \frac{Z_o}{R_g + Z_o}.$$

Thus, the characteristic impedance of the T.L.  $Z_o = R_g = 50 \text{ Ohm}$ .

- b) The plot has a jump at  $t = 2 \text{ ns}$ , and we can infer that it takes the wave  $2 \text{ ns}$  to start from the source, then get reflected by the defect, finally go back to the source. Based on this, we have

$$\frac{2d}{v} = 2 \text{ ns}.$$

Therefore,  $d = 0.2 \text{ m}$ .

- c) Again, from the plot we know the reflection coefficient at the defect is  $\Gamma_d = 1$  ( $(1 - 0.5)/0.5$ ). On the other hand, we have

$$\Gamma_d = \frac{(R_d + Z_o) - Z_o}{(R_d + Z_o) + Z_o} = \frac{R_d}{R_d + 2Z_o}.$$

where  $R_d$  denotes the effective series resistance of the defect. We see  $R_d$  should be very/infininitely large. So the defect is actually an open circuit.

- d) Since all the incident wave get reflected at the defect, there will be no voltage response at the load.