

1. A transmission line of length  $L = 5$  m and  $v = \frac{1}{3}c = 10^8$  m/s is open circuited at ends  $z = 0$  and  $z = L$ .

a) In general, the phasor voltage on the T.L. has the following form

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

and the corresponding phasor current is given by

$$I(z) = \frac{V^+}{Z_o} e^{-j\beta z} - \frac{V^-}{Z_o} e^{j\beta z}.$$

Because the ends of the T.L. are open circuited, the current phasors at these locations must be zero. Applying this condition at  $z = 0$  (i.e.,  $I(0) = 0$ ), we find that

$$V^+ = V^-.$$

At the other end, we have that  $I(L) = 0$ , and thus

$$V^+ e^{-j\beta L} - V^+ e^{j\beta L} = -V^+ 2j \sin(\beta L) = 0.$$

The non-trivial solutions of the previous equation (i.e., for  $V^+ \neq 0$ ) must satisfy  $\sin(\beta L) = 0$ , and therefore

$$\beta = \frac{n\pi}{L}$$


for any integer  $n$ . As a result the resonant frequencies  $f_n$  are simply

$$f_n = \frac{v}{\lambda} = \frac{\beta}{2\pi} v = \frac{n}{2L} v = n \frac{10^8}{2 \times 5} = 10 \cdot n \text{ MHz}.$$

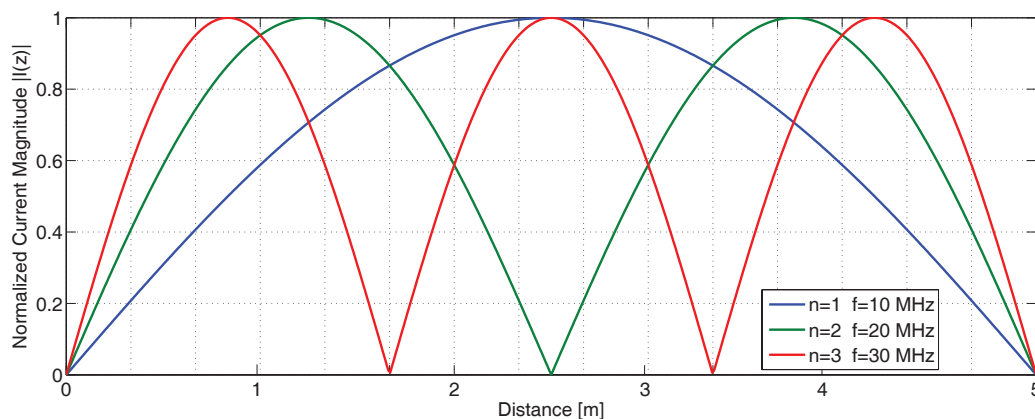b) The current on the T.L. for the  $n$ -th resonant frequency  $f_n$  is given by

$$I(z) = -2j \frac{V^+}{Z_o} \sin\left(\frac{n\pi}{L} z\right) \text{ A}.$$


The maximum magnitude of the current will be  $\frac{2V^+}{Z_0}$ , and the normalized figure :



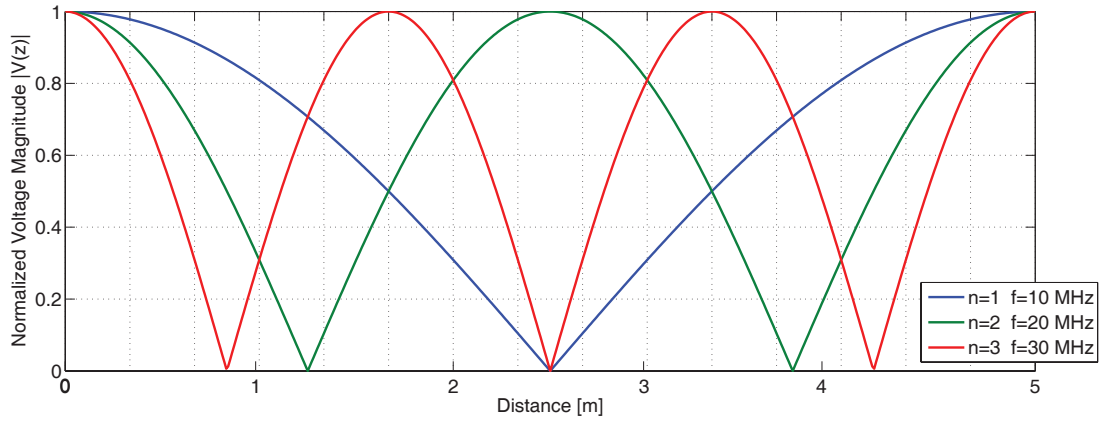c) We can also find that the voltage on the T.L. for the  $n$ -th resonant frequency  $f_n$  is given by

$$V(z) = 2V^+ \cos\left(\frac{n\pi}{L} z\right) V.$$

The maximum magnitude of the current will be  $2V^+$ , and the normalized figure :



2. By the steady state analysis, we can regard all components as general impedance. The impedance of the capacitor is

$$Z_C = \frac{1}{j\omega C}.$$

- (a) The input impedance of an open T.L. stub is

$$\begin{aligned} Z_{in} &= -jZ_o \cot(\beta l) \\ &= j5.255 \Omega \end{aligned}$$

- (b) According to the voltage split,

$$V_L = V_g \frac{R_L}{R_L + R_g + Z_{in} + Z_C}.$$

Since  $V_L = \frac{1}{2}V_g$  and  $R_L = R_g$ , we get  $Z_{in} + Z_C = 0$ . Therefore,

$$C = -\frac{1}{\omega Z_o \cot(\beta l)} = 606 \text{ pF}.$$

3. For this two TL case:

- For half-wave transform,  $V_{L1} = -V_{in} = -j10 \text{ V}$ .
- For quarter-wave transform,  $V_{in} = jI_{L2}Z_o = j\frac{V_{L2}}{Z_{L2}}Z_o$ . So  $V_{L2} = \frac{Z_{L2}}{Z_o}(-j)(j10) = 5 \text{ V}$ .
- $I_{L1} = \frac{V_{L1}}{Z_{L1}} = \frac{-j10}{200} = -j0.05 \text{ A}$ .
- $I_{L2} = \frac{V_{L2}}{Z_{L2}} = \frac{5}{50} = 0.1 \text{ A}$ .
- For half-wave transform:  $Z_{in1} = Z_{L1} = 200 \Omega$ ; For quarter-wave transform:  $Z_{in2} = \frac{Z_o^2}{Z_{L2}} = 200 \Omega$ . Combine in parallel:  
 $Z_{in} = (\frac{1}{Z_{in1}} + \frac{1}{Z_{in2}})^{-1} = 100 \Omega$ .
- $P = P_1 + P_2 = \frac{1}{2}\text{Re}\{V_{L1}I_{L1}^*\} + \frac{1}{2}\text{Re}\{V_{L2}I_{L2}^*\} = \frac{1}{4} + \frac{1}{4} = \frac{1}{2} \text{ W}$ .

4. The input impedance of a quarter-wavelength transformer is  $Z_{in} = \frac{Z_o^2}{Z_L}$ .

- Given that  $I_{in} = \frac{V_{in}}{Z_{in}} = \frac{Z_L}{Z_o^2}V_{in}$  and  $V_{in} = j\frac{V_L}{Z_L}Z_o$ ,  $V_L = -jI_{in}Z_o = -j50 \text{ V}$ .
- If the load end is short then  $V_L = 0$ . This implies that the current input must also be zero, and therefore,  $I_{in} = 0.5\angle 0^\circ \text{ A}$  is not a possibility in this situation.
- Given that  $I_{in} = \frac{V_{in}}{Z_{in}} = \frac{Z_L}{Z_o^2}V_{in}$  and considering  $Z_L = 50 \Omega$ , yields  $V_{in} = 100 \text{ V}$ .

5. We will use our knowledge of  $\lambda/2$  and  $\lambda/4$  transformers to solve this problem. Since the line connected to the generator is one wavelength long (i.e. two  $\lambda/2$  lines combined), the voltage and current at the junction of the three transmission lines are equal to the voltage and current at the generator ( $V_{in} = V_g$ ).

a) The voltage phasor at load  $R_{L1}$  will be

$$V_{L1} = -V_g = -100 = 100e^{j\pi} \text{ V},$$

and thus, the current phasor at load  $R_{L1}$  will be

$$I_{L1} = \frac{V_{L1}}{R_{L1}} = 2e^{j\pi} \text{ A}.$$

We know from problem 3 that load current in case of  $\lambda/4$  transformer is  $I_L = -j\frac{V_{in}}{Z_o}$ , thus the voltage phasor at load  $R_{L2}$  will be

$$V_{L2} = I_{L2}Z_{L2} = -j\frac{V_{in}}{Z_{o2}}R_{L2} = \frac{100}{50}50e^{-j\frac{\pi}{2}} = 100e^{-j\frac{\pi}{2}} \text{ V},$$

and thus, the current phasor at load  $R_{L2}$  will be

$$I_{L2} = \frac{V_{L2}}{R_{L2}} = 2e^{-j\frac{\pi}{2}} \text{ A}.$$

b) The power dissipated in resistor  $R_{L1}$  is

$$P_{L1} = \frac{1}{2}\text{Re}\{V_{L1}I_{L1}^*\} = \frac{1}{2}\text{Re}\left\{\frac{|V_{L1}|^2}{R_{L1}^*}\right\} = 100 \text{ W}.$$

Then examining the second line, we know that the  $\lambda/4$  transformer has a load current  $I_L = -j\frac{V_{in}}{Z_o}$ . Thus, the expression for the time average dissipated power in resistor  $R_{L2}$  is

$$P_{L2} = \frac{1}{2}\text{Re}\{V_{L2}I_{L2}^*\} = \frac{1}{2}\text{Re}\left\{100e^{-j\frac{\pi}{2}} \cdot 2e^{j\frac{\pi}{2}}\right\} = 100 \text{ W}.$$

6. The lossless TL has  $l = \lambda$  and  $Z_0 = 50 \Omega$

a)  $I_L = \frac{V_L}{Z_L} = \frac{-j10}{150} = -j\frac{1}{15} \text{ A}.$

b)  $Z(d) = Z_L$  for every  $\frac{\lambda}{2}$ , so at  $d = \frac{\lambda}{2}$  and  $d = \lambda$ .

c) For quarter-wave transform,  $V(\frac{\lambda}{4}) = jI_LZ_o = \frac{10}{3} \text{ V}$ , and  $I(\frac{\lambda}{4}) = j\frac{V_L}{Z_o} = \frac{1}{5} \text{ A}.$

d)  $Z(\frac{\lambda}{4}) = \frac{V(\frac{\lambda}{4})}{I(\frac{\lambda}{4})} = \frac{50}{3} \Omega.$

e) For half-wave transform,  $V(\frac{\lambda}{2}) = -V_L = j10 \text{ V}$ , and  $I(\frac{\lambda}{2}) = -I_L = j\frac{1}{15} \text{ A}.$

f) Since  $l = \lambda$ ,  $V_{in} = V_L = -j10 \text{ V}$ , and  $Z_{in} = Z_L = 150 \Omega$ ;

$$\begin{aligned} \frac{V_{in}}{V_g} &= \frac{Z_{in}}{Z_{in} + R_g} = \frac{-j10}{-j30} = \frac{1}{3} \\ R_g &= 2Z_{in} = 300 \Omega. \end{aligned}$$