
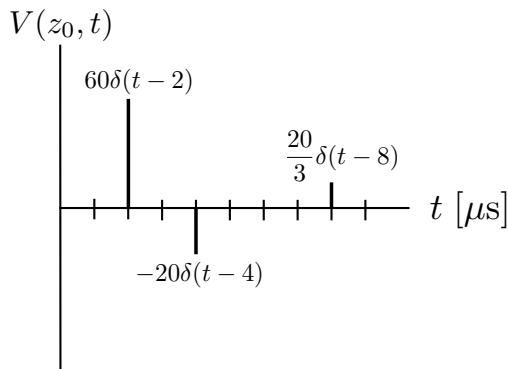


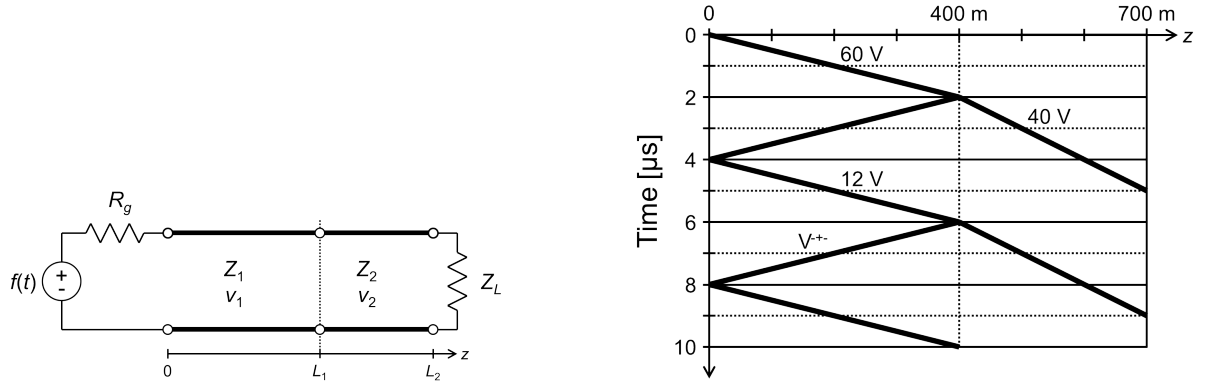1. Consider a T.L. with characteristic impedance $Z_o = 100 \Omega$, length $l = 600$ m, and propagation velocity $v = \frac{1}{\sqrt{LC}} = c = 3 \times 10^8$ m/s. A voltage source $f(t)$ with an internal resistance $R_g = Z_o$ is connected to one end of the T.L. (at $z = 0$) and the other end ($z = l$) is terminated by a load resistance $R_L = Z_o/2$.
 - a) Construct two “bounce diagrams” to determine the voltage, $V(z, t)$, and current, $I(z, t)$, variations on the line for $0 < z < l$ and $t > 0$ for $f(t) = \delta(t)$.
 - b) Write the expressions for $V(\frac{l}{4}, t)$ and $I(\frac{l}{4}, t)$ as weighted sums of appropriately delayed impulses $\delta(t)$.
 - c) Plot $V(\frac{l}{4}, t)$ as a function of t for $0 < t < 13 \mu\text{s}$ for $f(t) = 10u(t)$ V. — **Hint:** use the convolution of the result of part (b) with $30u(t)$.
 - d) Determine the steady state voltage and current on the line for the excitation from part (c).
2. A generator with internal resistance $R_g = 50 \Omega$ and an open circuit output voltage $f(t) = 90\delta(t)$ feeds a T.L. that has an unknown characteristic impedance Z_o and an unknown resistive load termination R_L at an unknown distance, L , from the generator. At a distance $z_0 = 300$ m from the generator, smaller than L , the voltage waveform as a function of time for $0 < t < 9 \mu\text{s}$ is found to be $V(z_0, t) = 60\delta(t - 2) - 20\delta(t - 4) + \frac{20}{3}\delta(t - 8)$ V, which is plotted below.




- a) Determine the injection coefficient τ_g and the impedance of the transmission line, Z_o .
- b) Determine the load reflection coefficient Γ_L and the load resistance, R_L .
- c) Determine the transmission time, $T = L/v_p$, of the impulse propagating on the transmission line.
- d) Determine the speed of wave propagation on the line, v_p , in m/s and the length of the transmission line, L in meters.
- e) Determine the next two voltage impulses (magnitudes and time delays) that will be measured at z_0 on the line for $t > 9 \mu\text{s}$.
- f) Sketch a bounce diagram for the *current* waveform $I(z, t)$ — not the voltage waveform as we have often done — for $0 < t < 12 \mu\text{s}$. Be sure to mark the numerical values for the amplitude of the current in the diagram.
- g) What is the algebraic expression for the current waveform as a function of (z, t) for the domain $0 < z < L$ and $0 < t < 12 \mu\text{s}$?

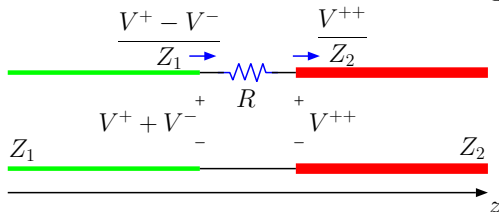3. A system of two transmission lines connected in series are driven by a voltage source $f_i(t) = V_0 u(t)$ and terminated by a resistive load of 60Ω as shown in the figure below. A switch is closed at $t = 0$ and the positive voltages are measured for $5\mu s$ giving the bounce diagram shown in the figure — the voltage values indicated in the diagram correspond to delta function weights times the source voltage V_0 , products such as $V_0\tau_g$, $V_0\tau_g(1 + \Gamma_{12})$, etc.




The impedance and transmission time of line 1 are Z_1 and T_1 and those of line 2 are Z_2 and T_2 . Using the figures, identify the following parameters in appropriate units:

- Transmission times T_1 and T_2
 - Propagation velocity v_{p1} on line 1, and propagation velocity v_{p2} on line 2
 - Impedance Z_2
 - Reflection coefficient Γ_{12} between lines 1 and 2
 - Impedance Z_1
 - Source resistance R_g
 - Source voltage V_0
 - Reflected voltage V^{+-} on line 1 (see the diagram for this notation)
 - Steady state voltage V_1 on line 1 as $t \rightarrow \infty$
 - Steady state voltage V_2 on line 2 as $t \rightarrow \infty$
4. Two T.L.'s with characteristic impedances Z_1 and Z_2 are joined at a junction that also includes a series resistance R as shown in the diagram below.



- Write the pertinent KVL and KCL equations at the junction that relate $V^+(t - \frac{z}{v_{p1}})$, $V^-(t + \frac{z}{v_{p1}})$ and $V^{++}(t - \frac{z}{v_{p2}})$.

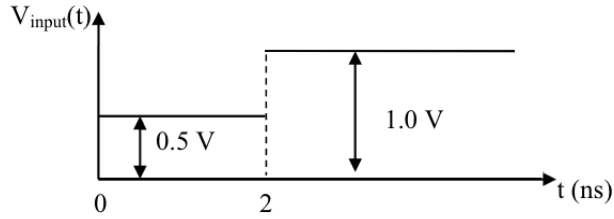- b) Solve the KVL and KCL equations above to obtain the reflection and transmission coefficients $\Gamma_{12} \equiv \frac{V^-}{V^+}$ and $\tau_{12} = \frac{V^{++}}{V^+}$ for the junction.
- c) Calculate $\Gamma_{12} \equiv \frac{V^-}{V^+}$ and $\tau_{12} = \frac{V^{++}}{V^+}$ for $Z_1 = 50 \Omega$, $Z_2 = 25 \Omega$, and $R = 100 \Omega$.
5. A defect in one of the wires of a transmission line manifests itself as an effective series resistance at a distance d from the input. The transmission line is lossless, of length 4 m, and propagation speed $v = 2 \times 10^8$ m/s. The load impedance is 50Ω . When the line is driven by a unit step voltage source with internal (Thevenin) source impedance of 50Ω , the voltage response at the input of the line, $V(0, t)$, is depicted in the figure below (where time is denoted in ns):



- a) Calculate the characteristic impedance of the transmission line;
- b) Calculate the distance d from the source where the defect occurs;
- c) Calculate the defect resistance;
- d) Plot the voltage response at the load.